

Designing a Lock-in Amplifier with Analog to Digital Conversion

Muir Morrison

Rachel Miller

Mike Gallaspy


Outline

- What is a lock-in? Why is it useful?
- Design & implementation of the analog circuit
- Digital electronics, very briefly
- Analog to digital conversion
- Concluding, and future work

Motivation & Lock-in Basics

- An example: measuring spectral response of LEDs, 10-100 μ V signal in few mV noise
- Possible with a lock-in, using phase-sensitive detection
- The key idea: make signal AC at known frequency, multiply waveforms

Lock-in Basics-Multiplying Sines

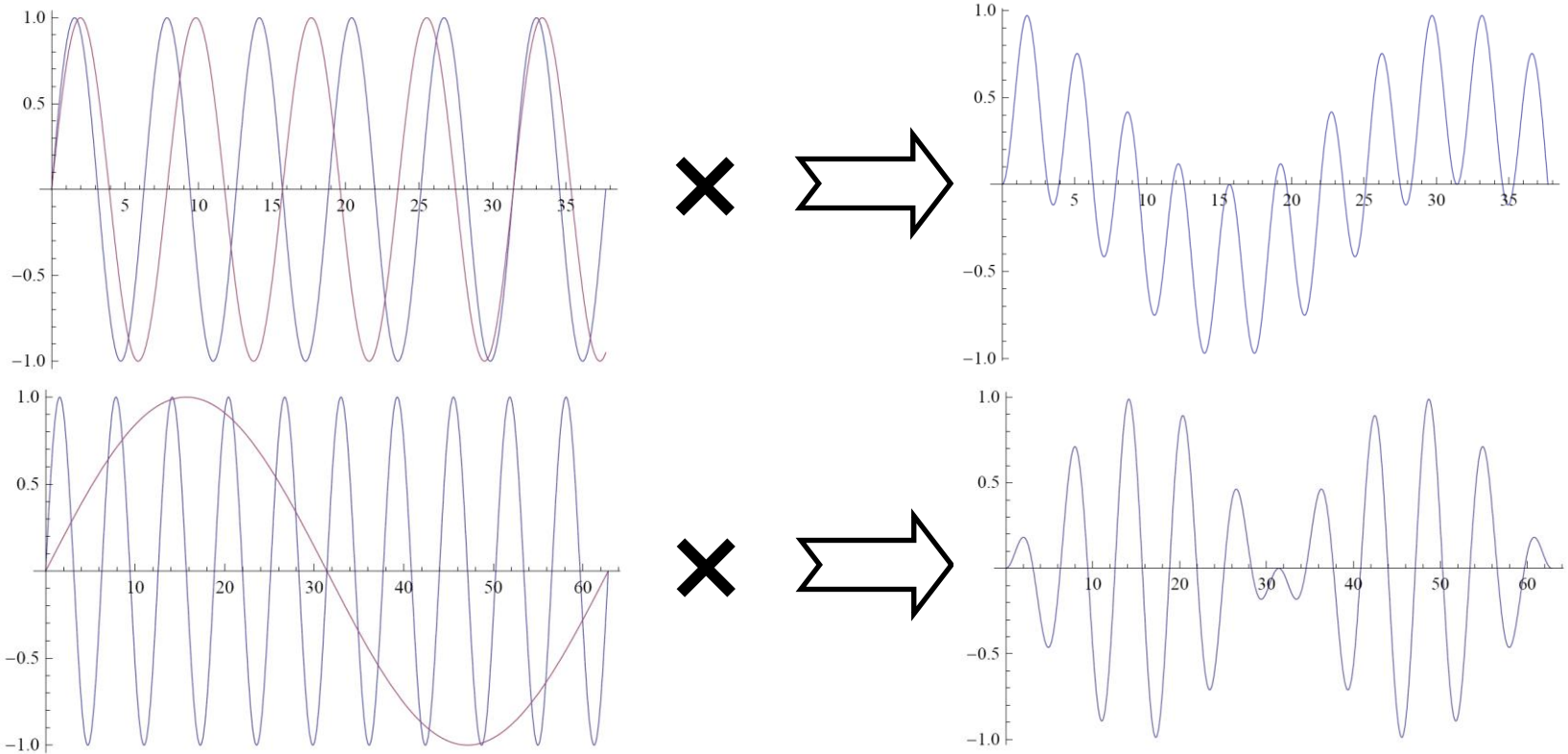


$$V_{\text{sig}} \sin(\omega_{\text{sig}} t) \times V_{\text{ref}} \sin(\omega_{\text{ref}} t) = 0.5 V_{\text{ref}} V_{\text{sig}} \cos(\omega_{\text{ref}} - \omega_{\text{sig}}) - 0.5 V_{\text{ref}} V_{\text{sig}} \cos(\omega_{\text{ref}} + \omega_{\text{sig}})$$

$$\text{if } \omega_{\text{ref}} = \omega_{\text{sig}}, \text{ then} \quad = 0.5 V_{\text{ref}} V_{\text{sig}} - 0.5 V_{\text{ref}} V_{\text{sig}} \cos(2\omega)$$


Retrieving the Signal

- Low pass filter: remove AC signals, DC remains, DC out is \propto input in
- Fourier Analysis: *any* signal can be written as sum/integral over frequencies, apply PSD to each component
- A narrow band-pass filter (easily get $Q \sim 10^5$ or more, compared to $Q \leq 100$)
- But what about phase?

Phase

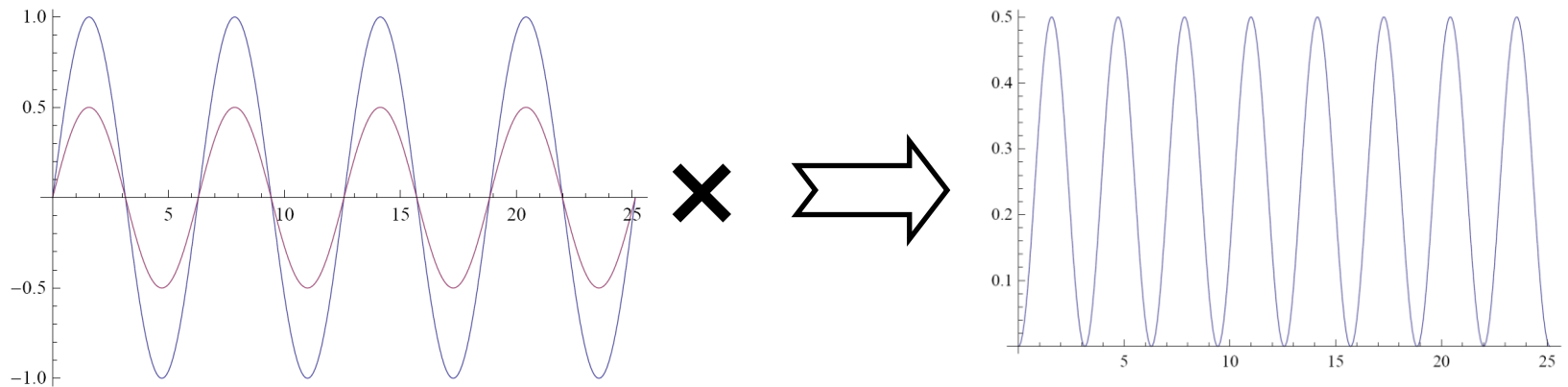


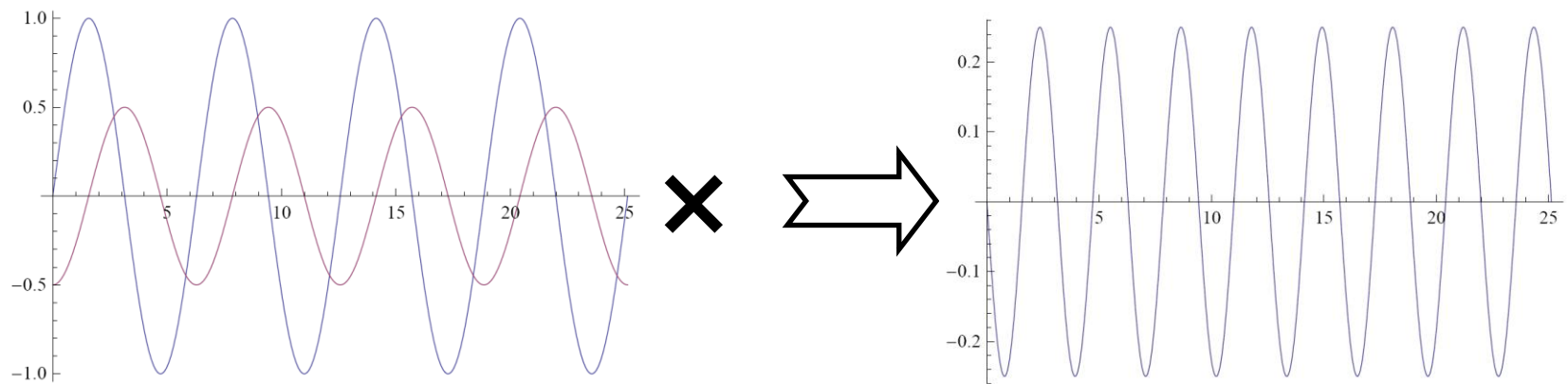
If signal and ref out of phase, DC signal vanishes on output!




In-Quadrature

- Solution: build a second lock-in, in parallel, with reference phase-shifted 90°
- Signal as a vector in complex space, where $X \leftrightarrow$ in-phase and $Y \leftrightarrow$ in-quadrature
- Magnitude: $R = \sqrt{X^2 + Y^2}$
- Phase: $\theta = \tan^{-1}(Y/X)$

Input Signal

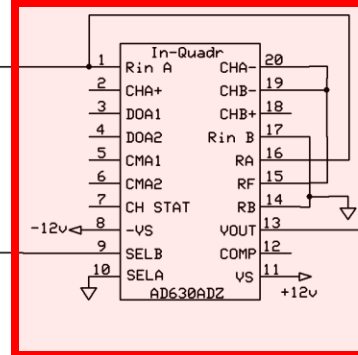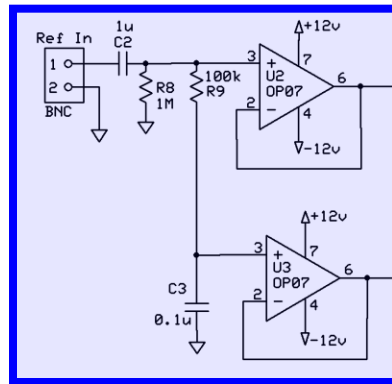


Demodulators

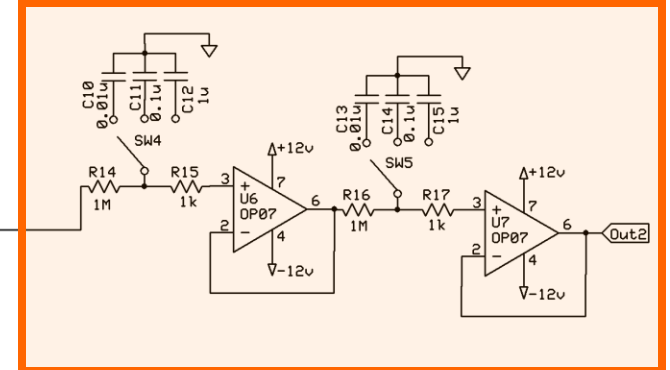


Low Pass Filters

ATMS 360		
Lock-in Amplifier		
	Rev 1.0 4/29/2010	Page 1 of 1

Input Stage

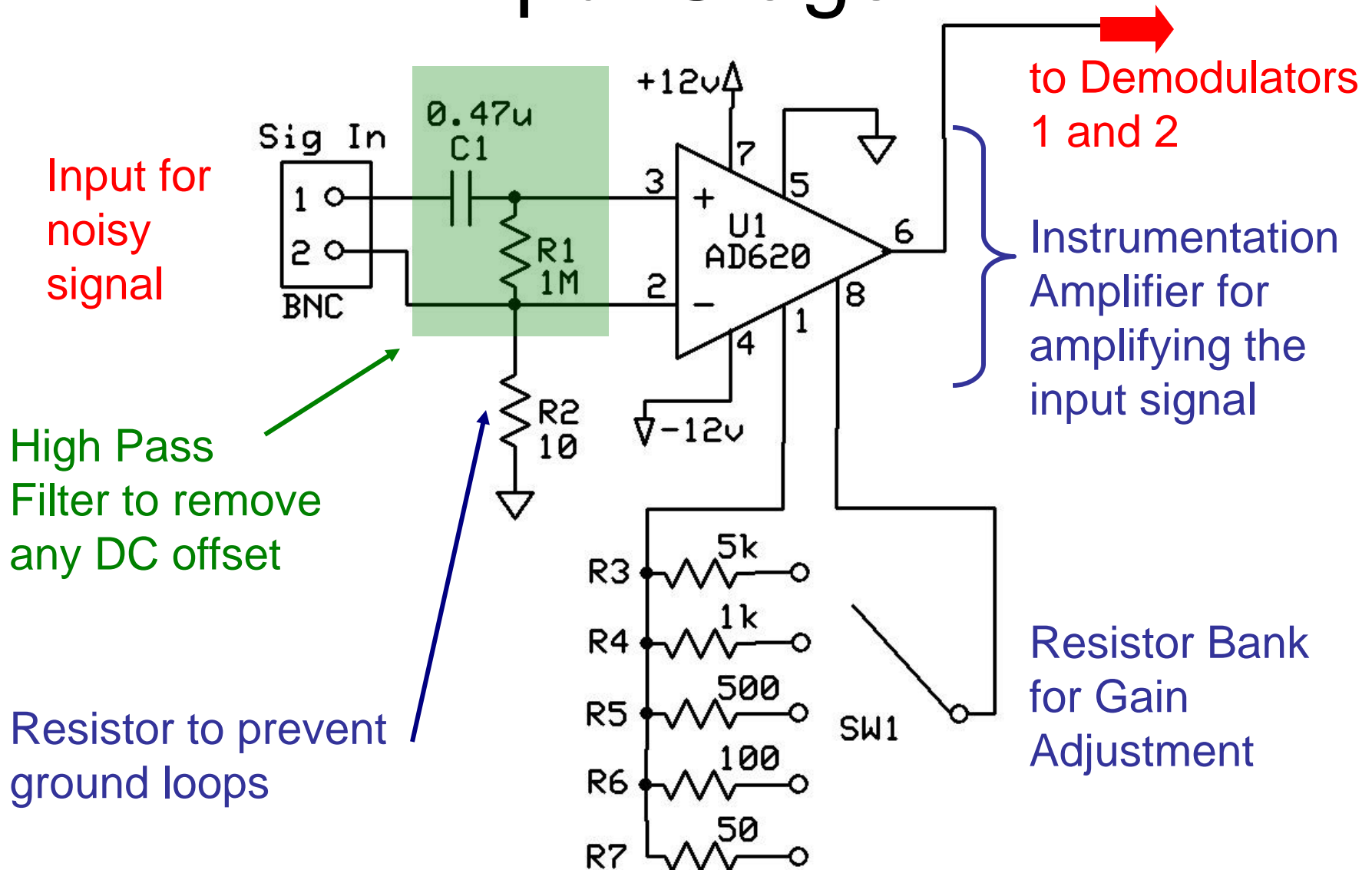

Ref Input and Phase-Shift Stage

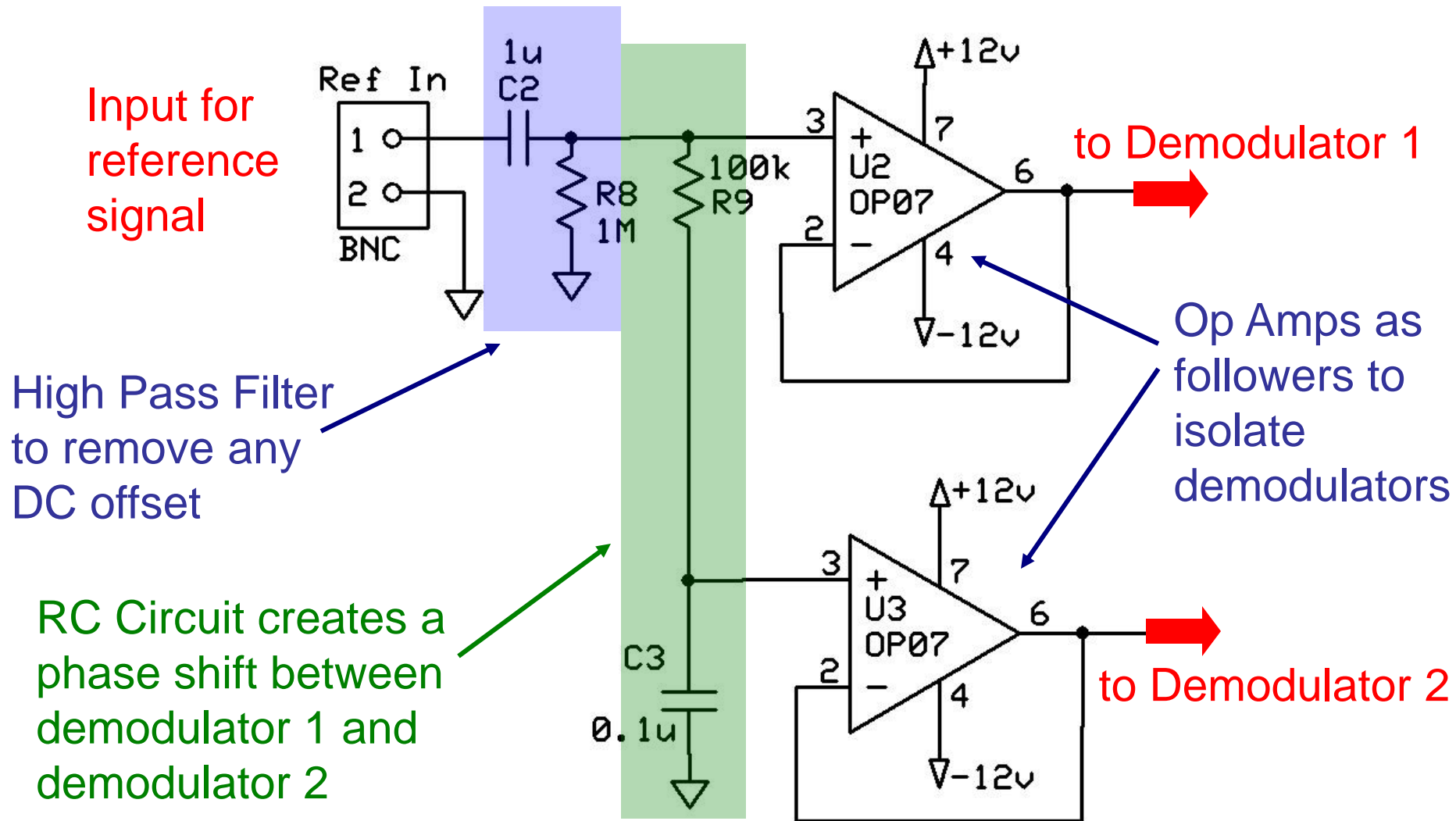

Phase Shift at Low Frequency

(noticeable below 500Hz for our setup)


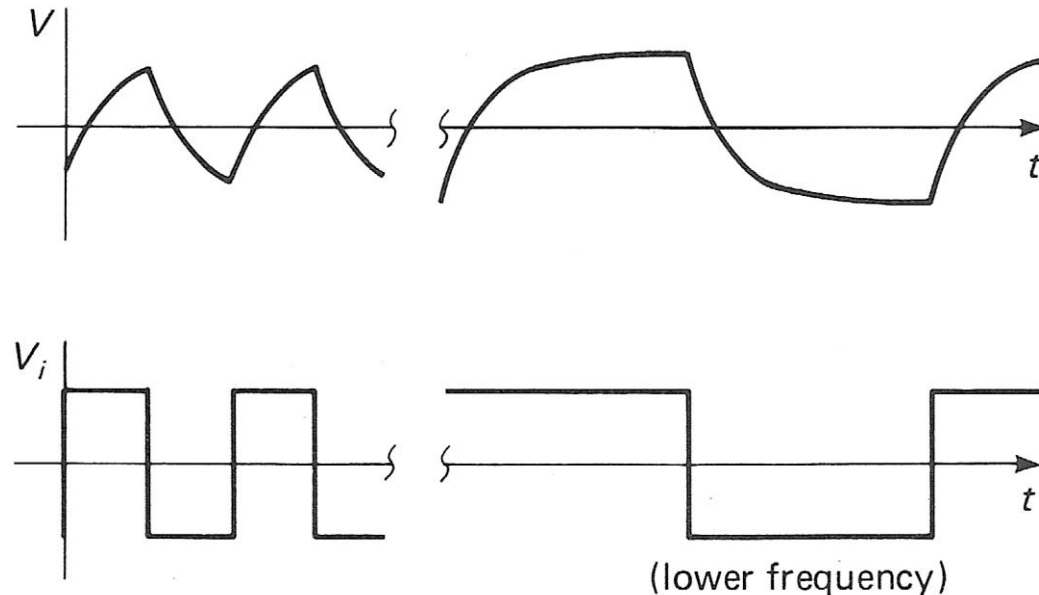



Figure 1.33. Output (top waveform) across a capacitor, when driven by square waves through a resistor.

At high frequencies (approx. above 500Hz), the signal approximates a triangle wave which can be used for the demodulator.


Demodulator: AD630

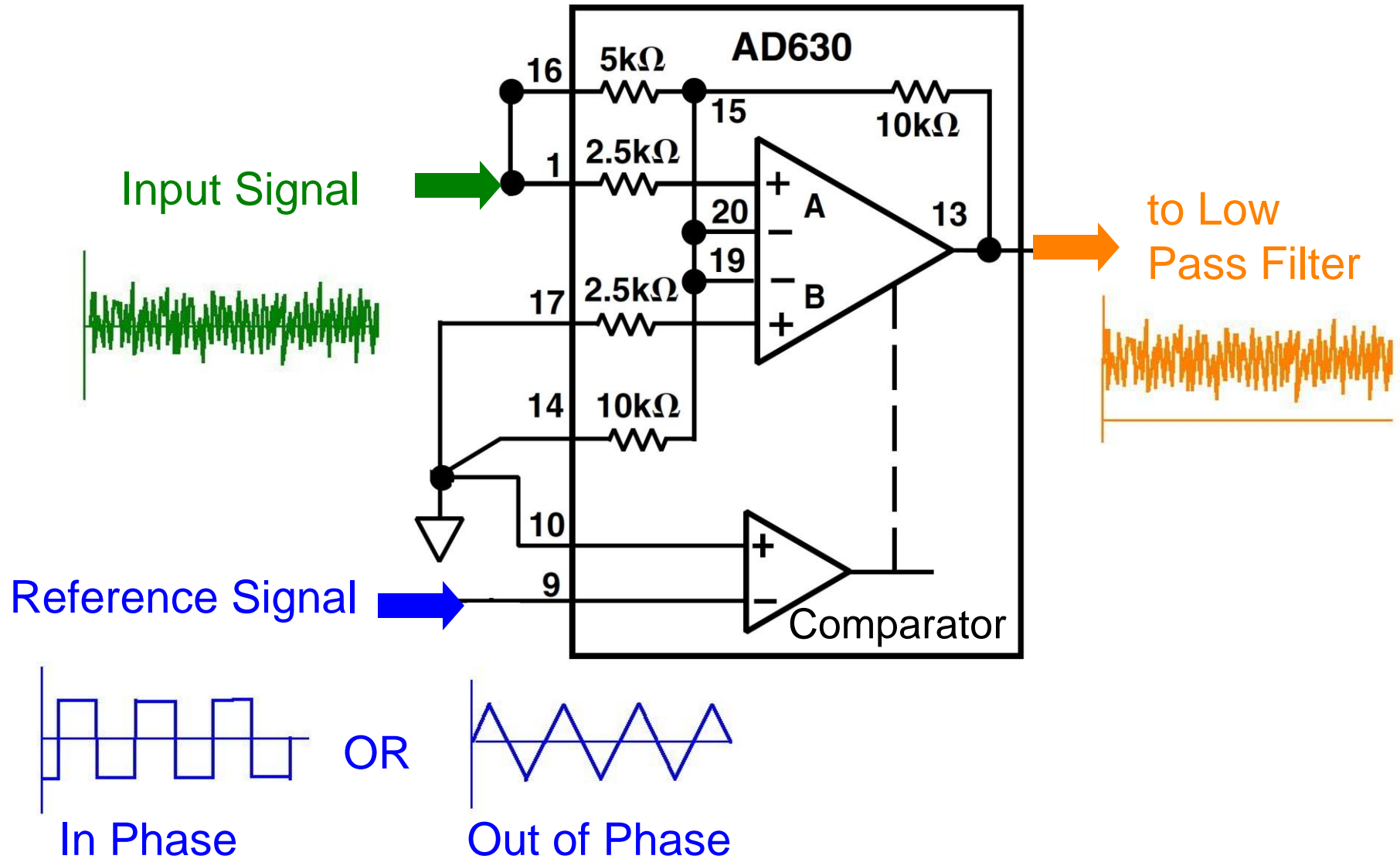

Low Pass Filter

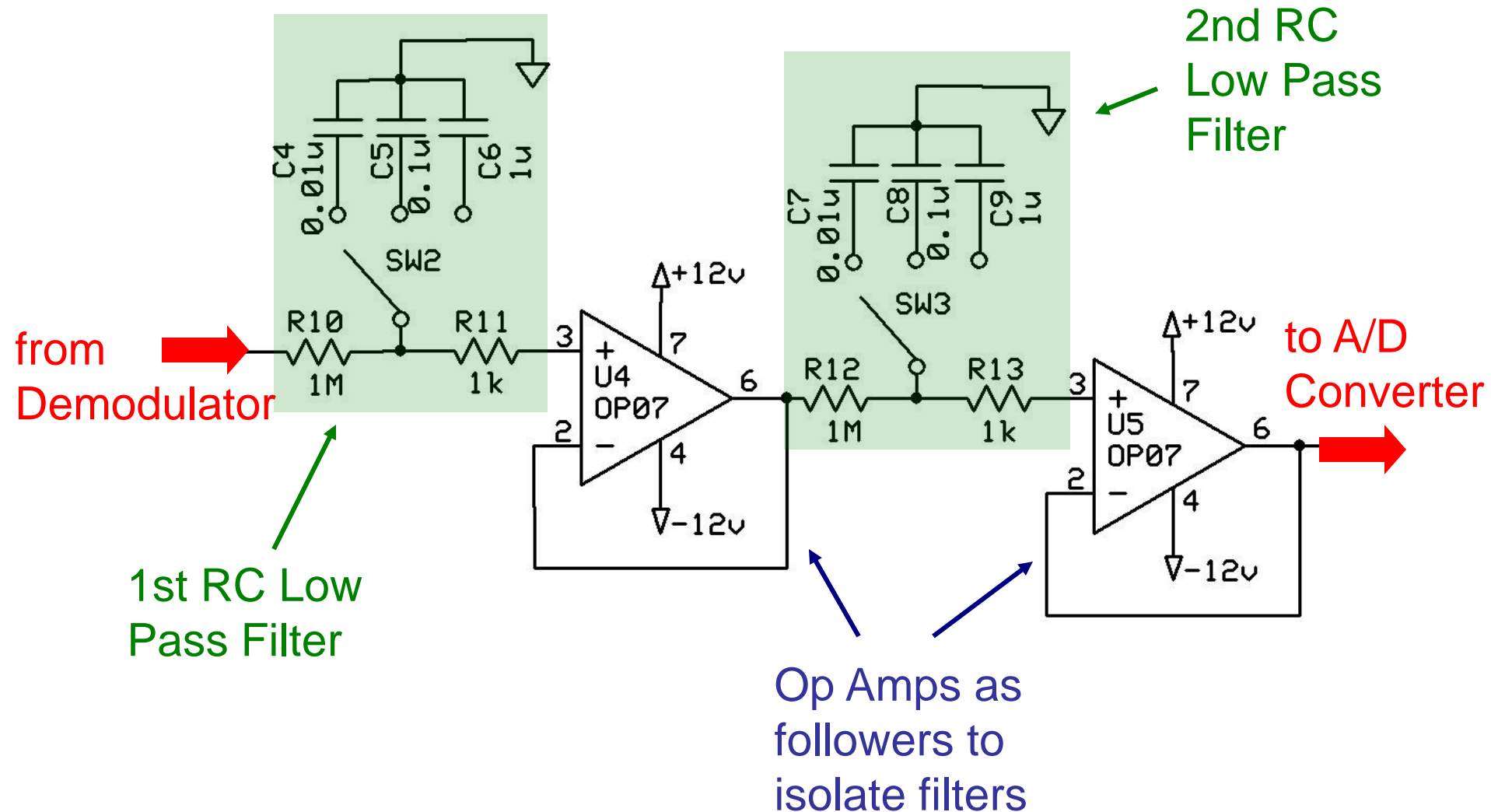

Rolloff of RC Low Pass Filters

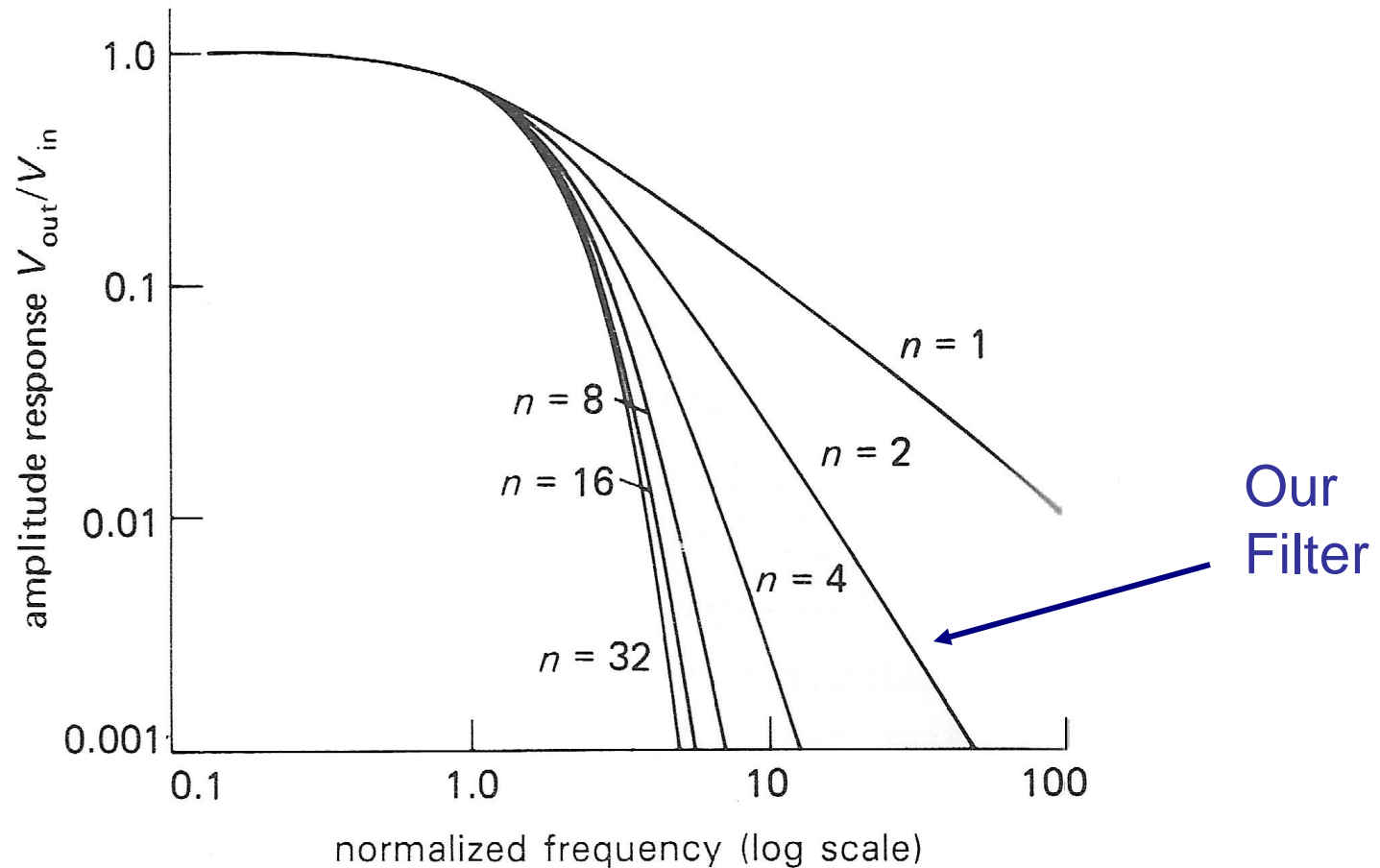



Input
Signal

Ref
Signal:
In Phase
+ Out of
Phase

Demodulators

Low
Pass
Filters

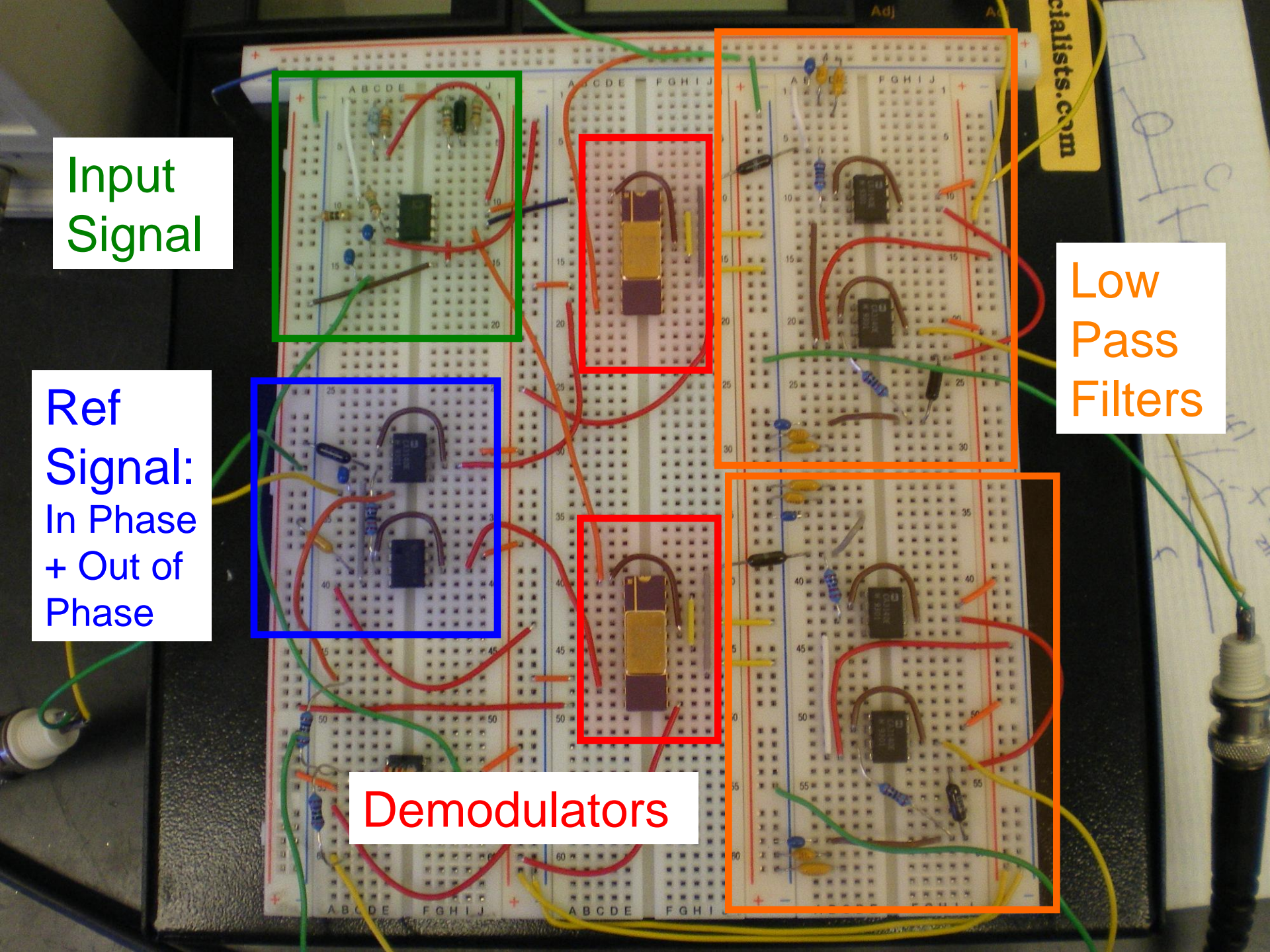

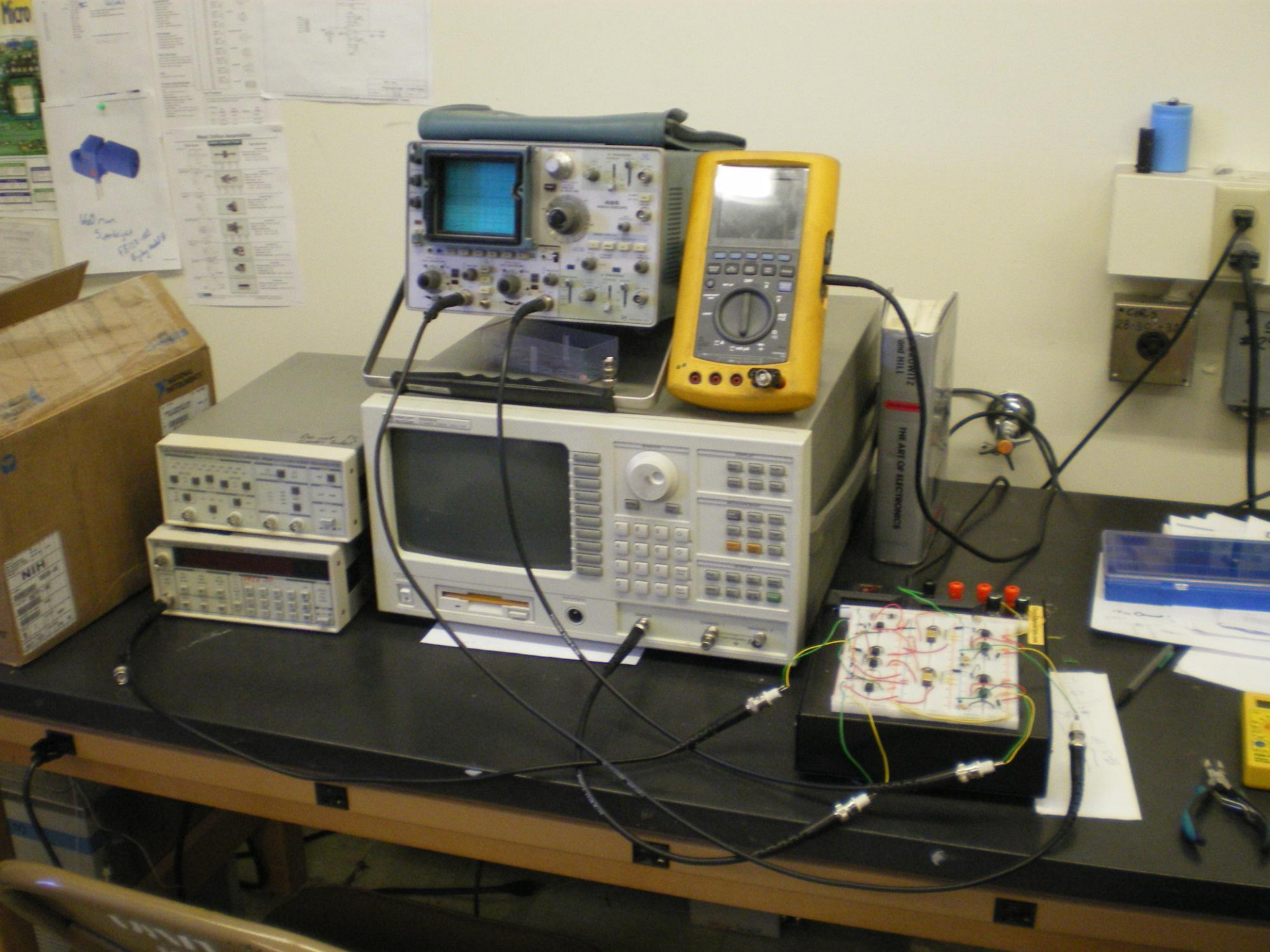



Digital Electronics

A fad?

Or the way of the future?

Analog vs. Digital

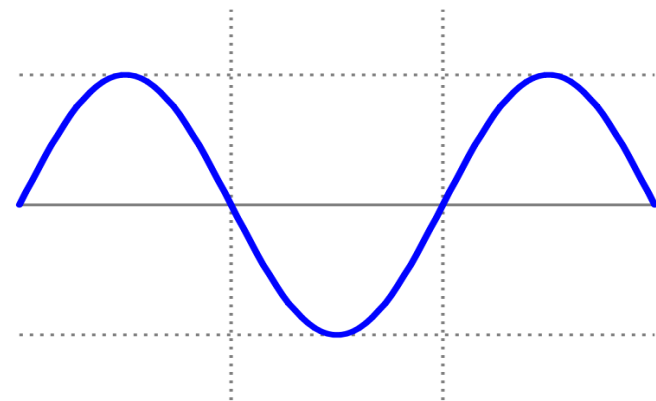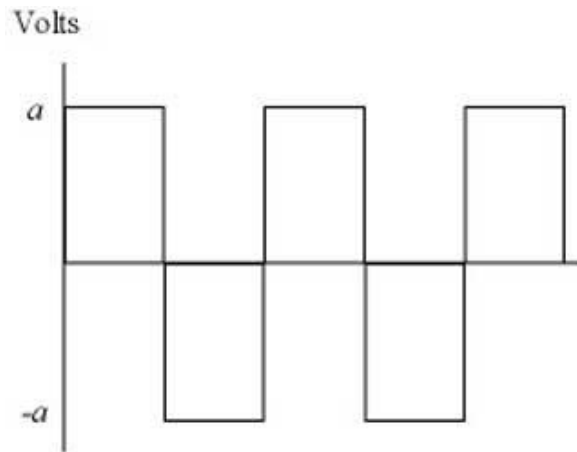- Analog responses (a voltage, for instance) are arbitrary functions of the input.
- A digital signal is either on or off... no intermediary state.



Digital Logic and Bits


- Digital electronics use digital logic...
 - One voltage (usually 5 or 3.3 volts) represents logic HIGH.
 - Another (usually ground, or slightly above ground) represents logic LOW.
- A bit is the fundamental unit of data for electronics.
 - It's either HIGH or LOW

Binary and Digital Data

- Binary numbers can be represented as a sequence of bits.
 - Each bit corresponds to a digit.
 - For each digit 1 = HIGH, 0 = LOW.
 - Thus 101 (binary) = $4 + 0 + 1 = 5$ (decimal)
- LTC 2440 stores digital conversion data in 24 place-value bits and one sign bit.

LTC 2440

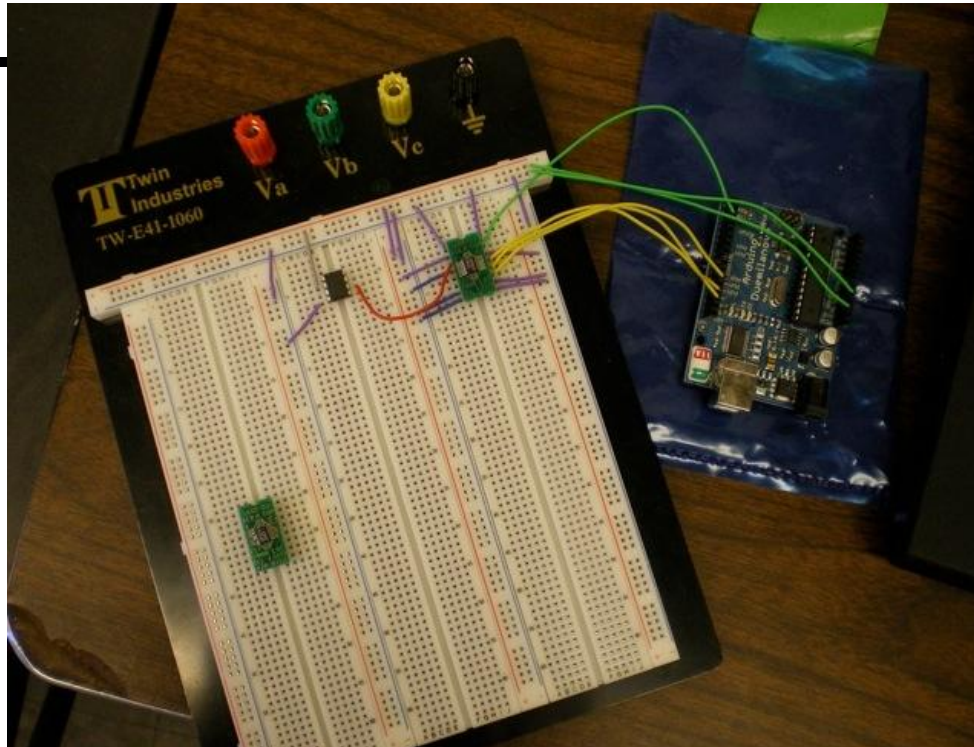- A little chip that converts an analog signal (a voltage) into a digital signal (a sequence of bits).



More on LTC 2440

- After powering on, the LTC 2440 converts an analog signal into a 24-bit integer, based off a reference signal.
 - There is a linear relationship between the reference signal and the full range of integers that 24 bits (plus a sign) can represent
- After conversion the LTC sits idle until it receives a clock pulse.
 - A clock is a dedicated digital channel that simply pulses on and off—this signals a change of state.
 - All processors are glorified clocks.
- At each clock pulse, one bit of data is shifted out.

Conclusion & Future Efforts

- Lock-in with $>60\text{dB}$ dynamic range, computer interfacing, wide bandwidth operation
- Low cost ($<\$100$ for components)
- Still to do
 - Computer controlled switches
 - Low-pass filters with sharper rolloff
 - Construction of actual PCB board
 - Case/housing
 - Further testing

References

- *SR830 Lock-in Amplifier Manual*. Stanford Research Systems. Sunnyvale, CA. (1993)
- Sengupta, S.K., J. M. Farnham, and J. E. Whitten. *A Simple Low-Cost Lock-In Amplifier for the Laboratory*. J. of Chem. Ed., Vol 82, No 9 (2005).
- Sonnaillona, M.O. and F. J. Bonettob. *A low-cost, high-performance, digital signal processor-based lock-in amplifier capable of measuring multiple frequency sweeps simultaneously*. Rev. Sci. Inst. 76, 024703 (2005).
- *AD620 Instrumentation Amplifier*. Analog Devices, Inc. Norwood, MA. (2004)
- *AD630 Balanced Modulator/Demodulator*. Analog Devices, Inc. Norwood, MA. (2004)
- *AD780 Precision Voltage Reference*. Analog Devices, Inc. Norwood, MA. (2004)
- *ADG411 Precision Quad SPST Switches*. Analog Devices, Inc. Norwood, MA. (2004)
- *LTC2440 24-Bit Analog-to-Digital Converter*. Linear Technology Corp. Milpitas, CA.
- Horowitz, P. and W. Hill. *The Art of Electronics*. Cambridge University Press,



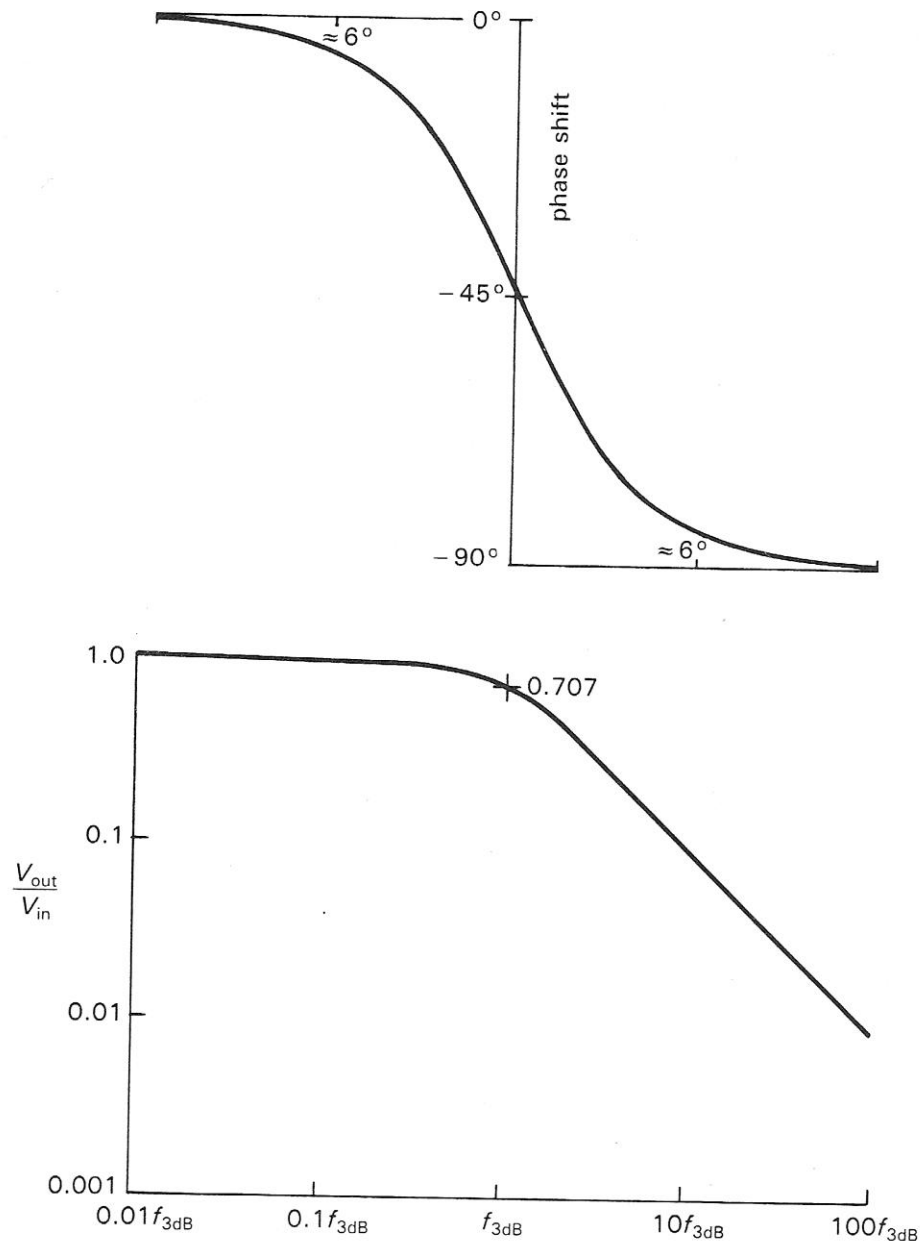


Figure 1.60. Frequency response (phase and amplitude) of low-pass filter, plotted on logarithmic axes. Note that the phase shift is 45° at the 3dB point and is within 6° of its asymptotic value for a decade of frequency change.

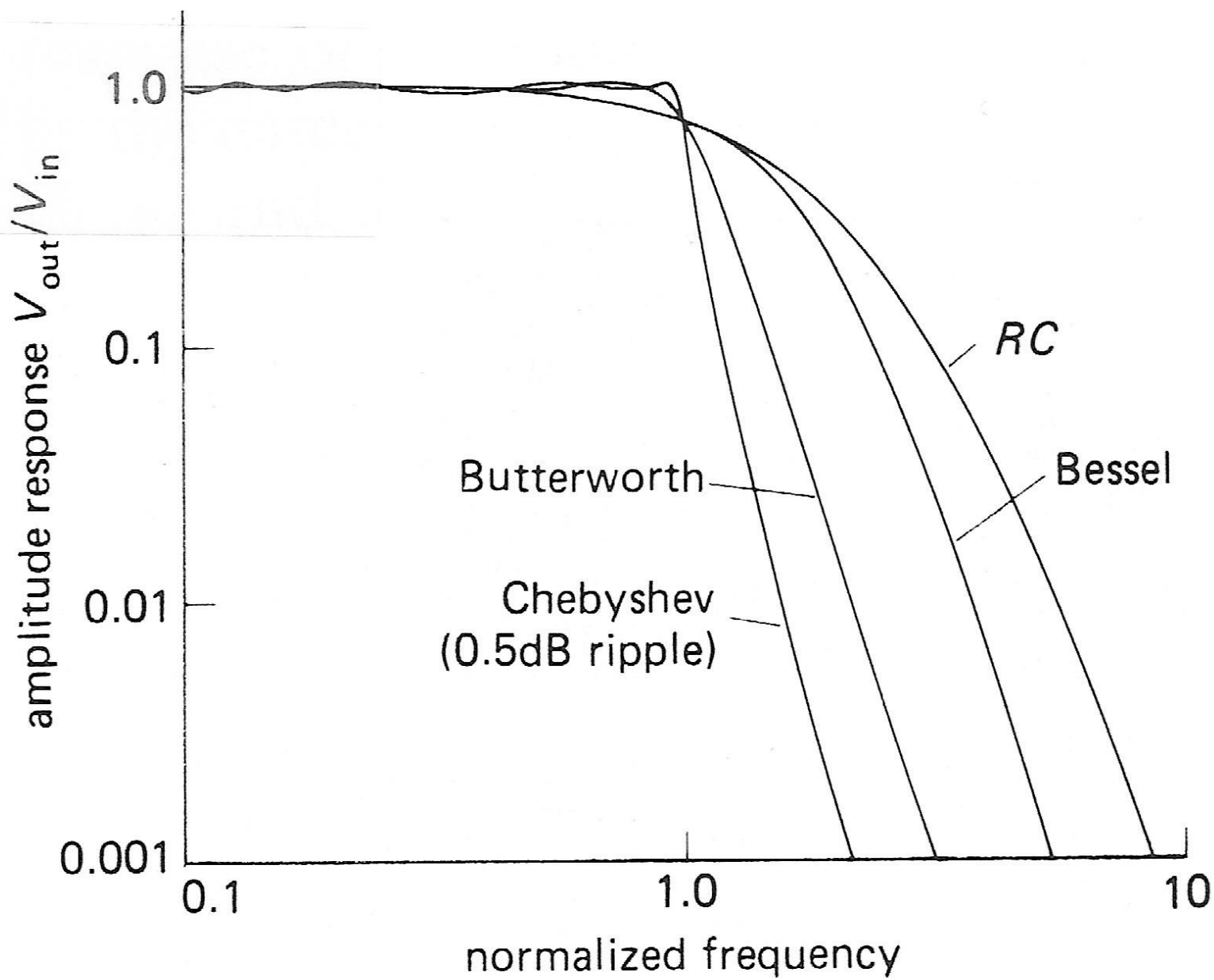

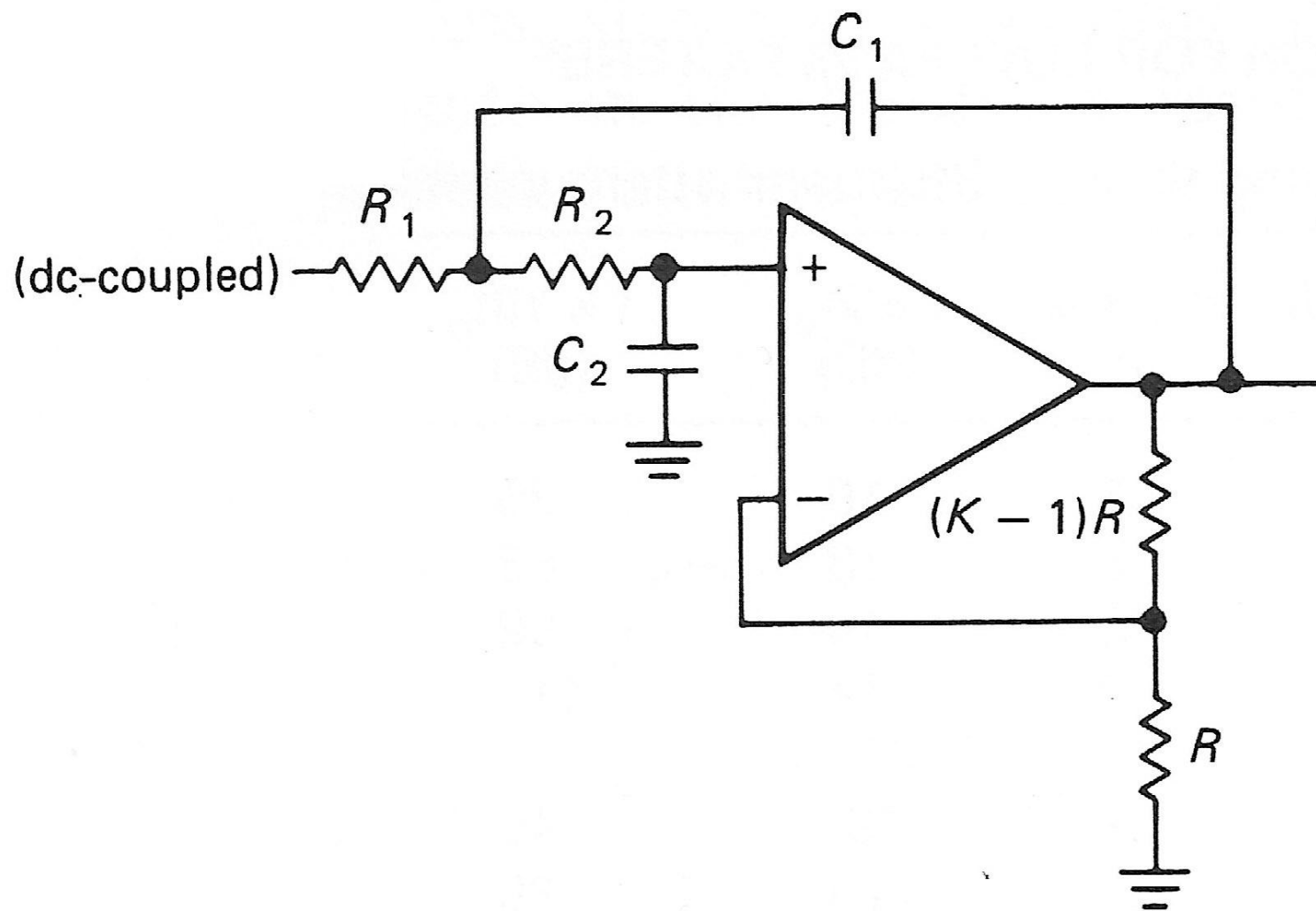

low-pass filter